

# #HW3 Cell Based Phased-Locked Loop Design report

## ◆ Group member

1. Department - ESS , Name - 林士登, ID : 110011207
2. Department - EE , Name - 陳立珩, ID : 110011222

## ◆ Contribution


1. 林士登 - Verilog code, Testbench, Synthesis, Layout testing and Simulations, Final summary report
2. 陳立珩 - Verilog code, Testbench, Synthesis, Layout testing and Simulations

## ◆ Outline

1. PLL Architecture
2. PLL waveform and frequency comparison (pre-layout / post-layout)
3. Functional cells in PLL
4. Gate-level synthesis / Gate simulation report
5. Layout generation and analysis

## ◆ Results and Analysis

### 1. PLL Architecture

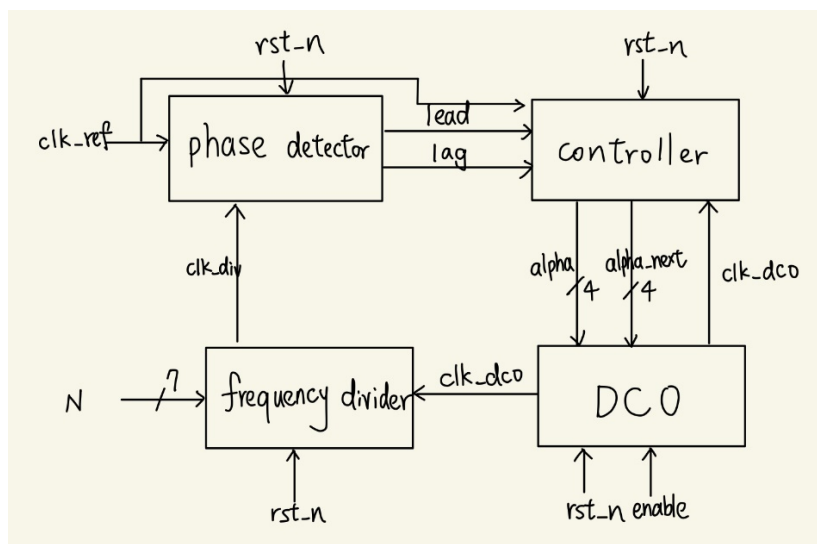


The graph indicated above represents our main PLL architecture. The main goal of the PLL is to achieve a 92MHz output clk signal with input reference clk of 1MHz. In addition to the general PLL design approach, we designed the controller and DCO more resilient to prevent the frequency divider from feeding in some glitch generated during the alpha code transition, the functional blocks and their corresponding function will be shown in the following part in our report (part 3.).

## 2. PLL waveform and frequency comparison

(‘PLL.v’ and ‘PLL\_tb.v’ code file is included in the submit area)


### Pre-sim

 

(entire timeline vs. frequency acquisition)

- ✓  $\alpha = 10$ , period = **10.848ns**, frequency = **92.183MHz**
- ✓  $\alpha = 11$ , period = **10.976ns**, frequency = **91.108MHz**
- ✓ The average clock cycle times of clk\_out observed over 10 clock cycles after the frequency acquisition is 10.848ns, the error compared to the ideal clock cycle time is  $|10.848 - 10.87| = \mathbf{0.022ns}$ , which is **0.2%** in percentage .

### Post-sim

 

(entire timeline vs. frequency acquisition)

- ✓  $\alpha = 6$ , period = **10.807ns**, frequency = **92.533MHz**
- ✓  $\alpha = 7$ , period = **10.941ns**, frequency = **91.399MHz**
- ✓ The average clock cycle times of clk\_out observed over 10 clock cycles after the frequency acquisition is 10.807ns, the error compared to the ideal clock cycle time is  $|10.807 - 10.87| = \mathbf{0.063ns}$ , which is **0.6%** in percentage .

Comparison of waveforms : The gate delays in post-layout is larger than those in pre-layout, which results in faster starting of frequency acquisition.

### 3. Functional cells in PLL

(phase\_detector.v / frequency\_divider.v / controller.v / DCO.v is included)



#### ① Phase detector

✓ **IO:**

Input: clk\_ref(clk), clk\_div(clk\_div), rst\_n(rst\_n)

Output: lead(lead), lag(lag)

✓ **Logic diagram:**

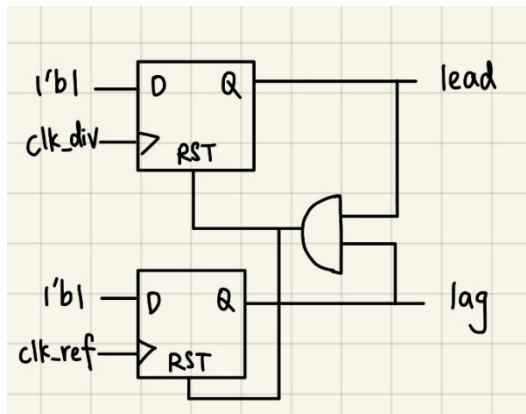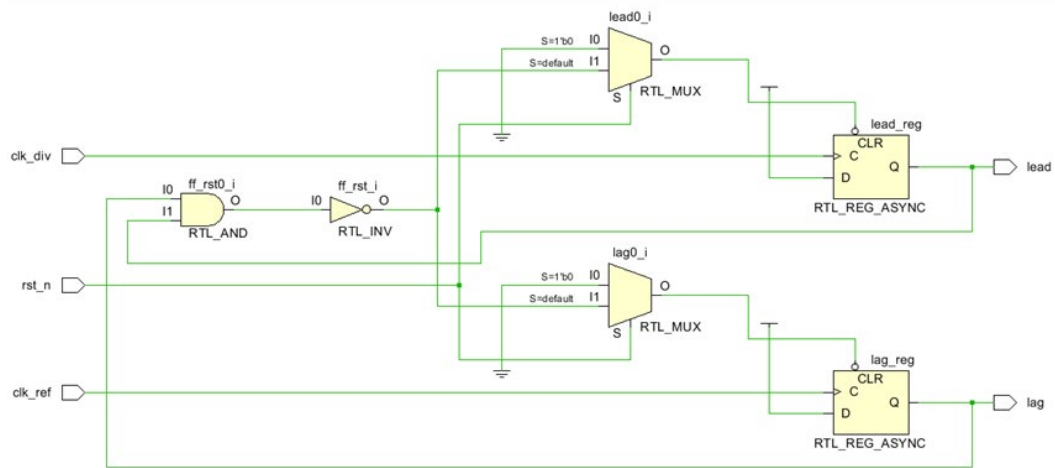

✓ **Operating mechanism:**

If clk\_div lags clk\_ref, then the phase detector produces a lag pulse. If clk\_div is ahead of clk\_ref, the phase detector produces a lead pulse. When both clk\_div and clk\_ref arrive, reset the lead and lag signals to 0.


② **Controller**

✓ **IO:**

Input: clk\_dco(clk\_dco), clk\_ref(clk\_ref), lead(lead), lag(lag), rst\_n(rst\_n)

Output: `alpha(alpha)`, `alpha_next(alpha_next)`

✓ **Logic diagram:**

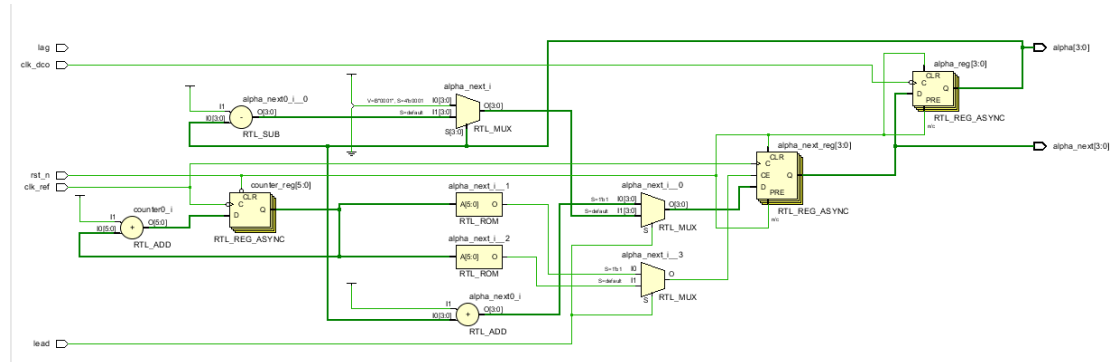

✓ **Operating mechanism:**

The controller is designed to detect the lead lag signal every 64 clk\_ref cycles (counter = 64). If clk\_div is ahead of clk\_ref (lead), the alpha\_next value will be incremented by 1. Otherwise, the alpha\_next value will be decremented by 1. In addition, we designed to pass alpha\_next to alpha when encountering clk\_dco negative edge (because we found that switching code at negative edge clk\_dco may eliminate glitches)


③ DCO

✓ **IO:**

Input: enable(enable), rst\_n(rst\_n),alpha(alpha),alpha\_next(alpha\_next)

Output: clk\_dco(clk\_dco)

✓ **Logic diagram:**

 

✓ **Operating mechanism:**

The design is as same in HW2, but in order to eliminate glitches, we deliberately switch the lambda code when  $\alpha == \alpha_{next}$ .



#### ④ Frequency divider

✓ **IO:**

Input: clk\_in(clk\_dco), rst\_n(rst\_n), N(N)

Output: clk\_out(clk\_div)

✓ **Logic diagram:**

 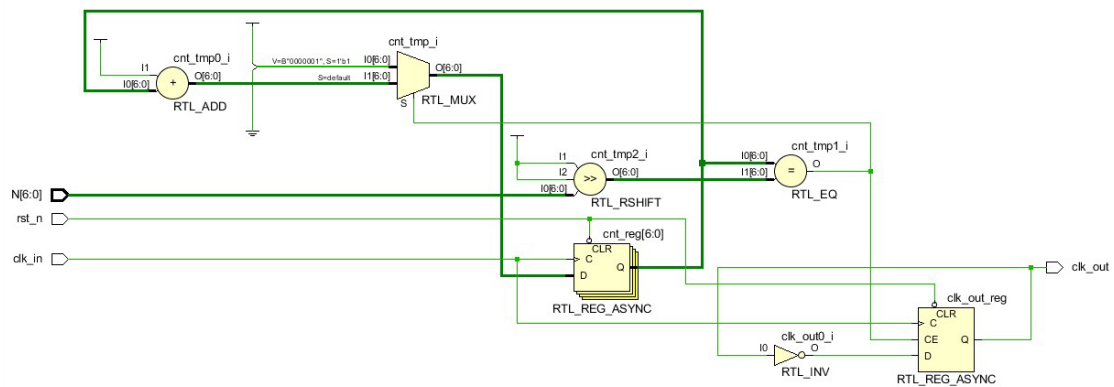

✓ **Operating mechanism:**

We designed a counter to calculate  $N/2$ , then declare a variable **cnt\_tmp**. If the value of counter is equal to  $N/2$ , reset the counter and continue the loop. Next, we designed a flip-flop with an input **clk\_tmp** and an output **clk\_out**, which changes ( $\sim \text{clk\_tmp}$ ) every  $N/2$  times. Finally, a clock with frequency of  $(\text{clk\_in})/N$  can be generated.

#### 4. Gate-level synthesis / Gate simulation report

##### Area Report

Combinational area: 913.046416  
Buf/Inv area: 491.803210  
Noncombinational area: 1157.889605  
Macro/Black Box area: 0.000000  
Net Interconnect area: undefined (No wire load specified)

Total cell area: 2070.936021  
Total area: undefined

- ① The total area shown in the 'PLL\_syn.report' file is 2070.936021  $\mu\text{m}^2$ .
- ② The number of final gate count is  $2070.936021 / 2.8224 = 733.75$ .


##### Power Report

Power Group	Internal Power	Switching Power	Leakage Power	Total Power	( % )	Attrs
io_pad	0.0000	0.0000	0.0000	0.0000	( 0.00%)	
memory	0.0000	0.0000	0.0000	0.0000	( 0.00%)	
black_box	0.0000	0.0000	0.0000	0.0000	( 0.00%)	
clock_network	0.0000	0.0000	0.0000	0.0000	( 0.00%)	
register	1.5906e-02	2.1521e-04	5.9499e+05	1.6716e-02	( 12.98%)	
sequential	2.6711e-02	6.3730e-05	2.3286e+06	2.9104e-02	( 22.60%)	
combinational	5.1189e-02	2.4078e-02	7.6650e+06	8.2932e-02	( 64.41%)	
Total	9.3806e-02 mW	2.4357e-02 mW	1.0589e+07 pW	0.1288 mW		

- ① Cell Internal Power = 93.806  $\mu\text{W}$  (74%)
- ② Net Switching Power = 24.357  $\mu\text{W}$  (26%)
- ③ Total Dynamic Power =  $93.806 + 24.357 = 118.163 \mu\text{W}$  (100%)
- ④ Cell Leakage Power = 10.589  $\mu\text{W}$
- ⑤ Total Power = 0.1288 mW


#### 5. Layout generation and analysis

##### Physical view

 



Amoeba view

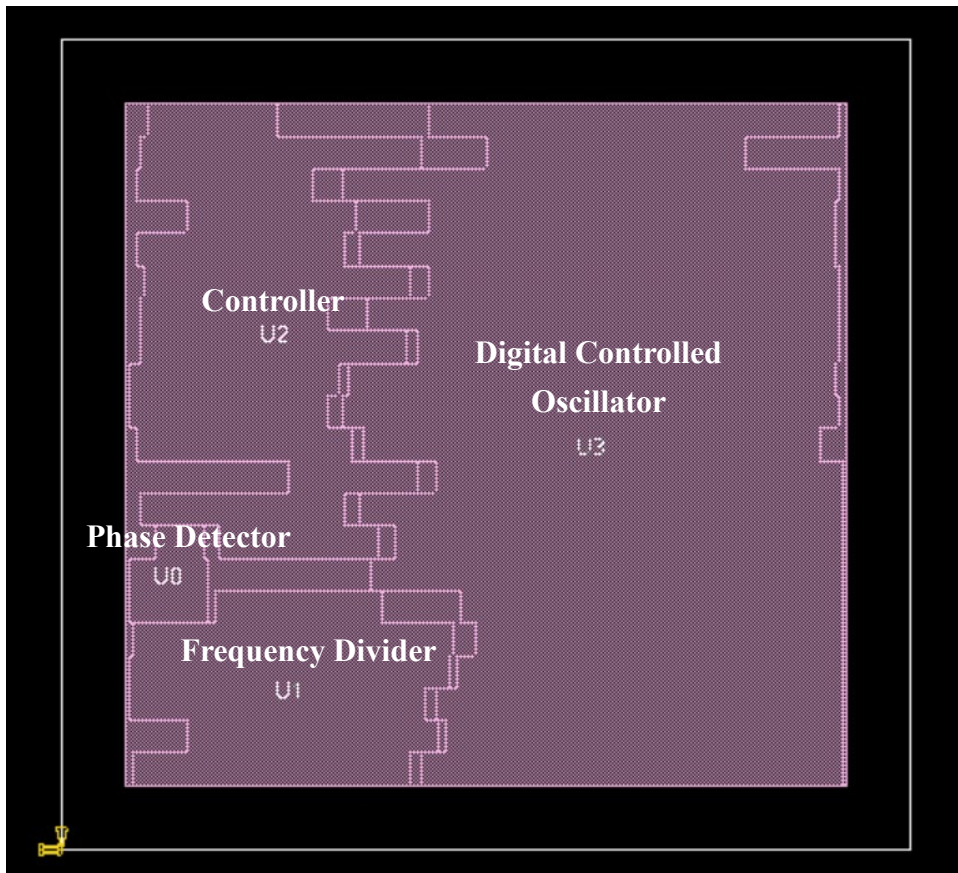

## Area Report

Layout total area = 2075.170  $\mu\text{m}^2$ .

```
innovus 2> report_area
```

Hinst Name	Module Name	Inst Count	Total Area
PLL		241	2075.170
U0	phase_detector	4	38.808
U1	frequency_divider	31	258.250
U1/add_18_aco	frequency_divider_DW01_inc_0_DW01_inc_2	7	60.682
U2	controller	43	461.462
U3	DCO	163	1316.650

## Power Report

Total Power		
Total Internal Power:	0.07820970	76.5267%
Total Switching Power:	0.01688925	16.5258%
Total Leakage Power:	0.00710033	6.9475%
Total Power:	0.10219927	

1. Total Internal Power = 0.07820970 mW
2. Total Switching Power = 0.01688925 mW
3. Total Leakage Power = 0.00710033 mW
4. Total Power = 0.10219927 mW